Study at School (Ignore the internal R in Dry Cell) Dry Cells and a Miniature bulb



RFAnalog Labs ©RFAnalog All Rights reserved Jan.23, 2012

Study at School (Consider the internal r in Dry Cell) Use Thevenin's theorem)



I represent a cullent flow in the dry cell. r0 represent internal resistance in a dry cell. E0 represent Electro-motive force in a dry cell. Parallel dry cell side , using Thevenin's theorem, it be changes. $I = E_0/(\Gamma_0/2+R_L)$

On any conditions, the current of a dry cell becomes half. ??

RFAnalog Labs ©RFAnalog All Rights reserved Jan.23, 2012



©RFAnalog All Rights reserved





The difference between an analog, **REALCOS** digital ones, and RF Physicochemically measurable things, such as sound, electricity and electromagnetic

waves (an electric wave, light, and radiation), frequency, heat, time, space, and gravity, or the thing decided by human feeling, such as a hobby and an idea, liking, a

Analog

REALUTION

Change of a limited and complicated continuous quantity is expressed.

Digital

Change of a limited and infinite

discontinuous quantity is expressed.

RF(Radio Frequency)

Continuation in limited and infinite time and frequency space and change of a discontinuous quantity are denoted by a comparatively simple waveform.

RFAnalog Labs ©RFAnalog All Rights reserved



Jan.23, 2012